

1.a)

```
entity parity_gen is
    -- this entity will be generic with n=7
    generic (n: integer := 7);
    -- the input signal is defined at compilation
    -- where n is an integer defined before
    port (input : in bit_vector (n-1 downto 0);
          output : out bit_vector(n downto 0));
end entity;

-- entering the architecture part of the code
architecture myarch of parity_gen is
    -- there are no internal signals defined here
begin
    -- entering process whose instructions are executed sequentially
    -- inside it. this process will be entered whenever input
    -- changes
    process(input)
        -- defining a bit variable
        variable temp1 : bit;
        -- defining a bit_vector variable whose size is the same as
        -- the the range of the output
        variable temp2 : bit_vector (output'range);
    begin
        -- initializing the temp variable to zero
        temp1:='0';
        -- loop that starts at i, and ends up at n-1
        for i in input'range loop
            -- XOR each individual element with the content
            -- of the temp variable, and store its result in
            -- there
            temp1 := temp1 XOR input(i);
            -- copy each input element to a temporary variable
            temp2(i) := input(i);
        end loop;
        temp2(output'high):=temp1; -- sets the parity as LSB bit
        output<=temp2; -- assigns the temporary value to the output
    end process;
end architecture;
```

I.b) Main program:

```
entity parity_gen is
    generic (n: integer := 4);
    port (input : in bit_vector (n-1 downto 0);
          output : out bit_vector(n downto 0));
end entity;

architecture myarch of parity_gen is
begin
    process(input)
        variable temp1 : bit; variable temp2 : bit_vector (output'range);
    begin
        temp1:='0';
        for i in input'range loop
            temp1 := temp1 XOR input(i); temp2(i) := input(i);
        end loop;
        temp2(output'high):=temp1;
        output<=temp2;
    end process;
end architecture;
```

Test-bench:

```
entity testparity is
end;

architecture bench of testparity is
    constant n : positive := 4;
    component parity_gen
        generic (n: integer := n);
        port (input : in bit_vector (n-1 downto 0);
              output : out bit_vector(n downto 0));
    end component;

    signal input  : bit_vector (n-1 downto 0);
    signal output : bit_vector(n downto 0);

begin

    input  <= "0000"
    , "0001" after 5 ns
    , "0010" after 10 ns
    , "0011" after 15 ns
    , "0100" after 20 ns ;

    m: parity_gen generic map(n) port map (input,output);

end bench;
```

Name	Value	S...	5	10	15	20	25
input	0100		0000	0001	0010	0011	0100
output	10100		00000	10001	10010	00011	10100

2.

```
SIGNAL a : BIT := '1';
SIGNAL b : BIT_VECTOR (3 DOWNTO 0) := "1100";
SIGNAL c : BIT_VECTOR (3 DOWNTO 0) := "0010";
SIGNAL d : BIT_VECTOR (7 DOWNTO 0);
SIGNAL e : INTEGER RANGE 0 TO 255;
SIGNAL f : INTEGER RANGE -128 TO 127;
```

a)

```
x1 <= a & c;          ->   x1 <= _____
x2 <= c & b;          ->   x2 <= _____
x3 <= b XOR c;        ->   x3 <= _____
x4 <= a NOR b(3);     ->   x4 <= _____
x5 <= b sll 2;        ->   x5 <= _____
x6 <= b sla 2;        ->   x6 <= _____
x7 <= b rol 2;        ->   x7 <= _____
x8 <= a AND NOT b(0) AND NOT c(1); ->   x8 <= _____
d <= (5=>'0', OTHERS=>'1'); ->   d <= _____
```

```
x1 <= "11100";
x2 <= "00101100";
x3 <= "1110";
x4 <= '0';
x5 <= "0000";
x6 <= "0000"; * sla means shift left arithmetic (fill right vacated bits with rightmost bit)
x7 <= "0011"; * rol mean rotate left (circular)
x8 <= '0';
d <= "11011111";
```

b)

c'LOW	->	<u>0</u>
d'HIGH	->	<u>7</u>
c'LEFT	->	<u>3</u>
d'RIGHT	->	<u>0</u>
c'RANGE	->	<u>(3 downto 0)</u>
d'LENGTH	->	<u>8</u>
c'REVERSE_RANGE	->	<u>(0 to 3)</u>

c)

b(0) AND a	• legal since both signals have the same data-type and dimensions
a + d(7)	• illegal arithmetic with bit datatype
NOT b XNOR c	• legal, logic operators amongst same sized bit_vectors
c + d	• illegal, arithmetic with bit_vector
e - f	• legal, arithmetic with integers is valid
IF (b<c) ...	• legal, comparing the same data types is okay
IF (b>=a) ...	• illegal, we are comparing two signals with different sizes
IF (f/=e) ...	• legal, valid comparison amongst same data types
IF (e>d) ...	• illegal, comparing different datatypes
b sra 1	• legal, shifting a bit_vector
c srl -2	• legal, shifting a bit_vector
f ror 3	• illegal, shifting a integer
e*3	• legal, multiplying a integer
5**5	• legal exponential operation
f/4	• legal, division with integers
e/3	• legal, division with integers
d <= c	• illegal, there is a size mismatch
d(6 DOWNT0 3) := b	• legal, size and data-type matches
e <= d	• illegal, operation with two different data-types
f := 100	• legal assignment as 100 is within the valid range

3.a) Main code:


```
library IEEE;
use ieee.std_logic_1164.all;

entity decoder is
    port (ena: in std_logic;
          sel: in std_logic_vector (2 downto 0);
          x : out std_logic_vector (7 downto 0)
    );
end decoder;

architecture generic_decoder of decoder is
begin
    process (ena,sel)
        variable temp1 : std_logic_vector(x'high downto 0);
        variable temp2 : integer range 0 to x'high;

    begin
        temp1:= (OTHERS => '1');
        temp2:=0;
        if (ena='1') then
            for i in sel'range loop
                if (sel(i)='1') then
                    temp2:=2*temp2+1;
                else
                    temp2:=2*temp2;
                end if;
            end loop;
            temp1(temp2):='0';
            end if;
            x<=temp1;
        end process;
    end architecture;
```

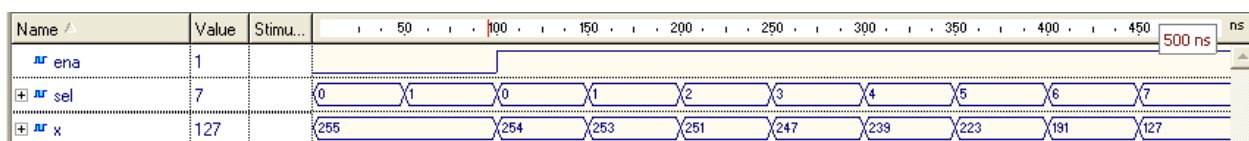Output-waveform generated by the test-bench on the next page:



Test-bench:

```
library IEEE;
use ieee.std_logic_1164.all;

entity testdecoder is
end;

architecture bench of testdecoder is
  component decoder
    port (ena: in std_logic;
          sel: in std_logic_vector (2 downto 0);
          x : out std_logic_vector (7 downto 0)
        );
  end component;

  signal ena   : std_logic;
  signal sel   : std_logic_vector (2 downto 0);
  signal x     : std_logic_vector (7 downto 0);

begin

  ena   <= '0', '1' after 100ns;
  sel   <= "000"           --0
  , "001" after 50ns       --1
  , "000" after 100ns      --0
  , "001" after 150ns      --1
  , "010" after 200ns      --2
  , "011" after 250ns      --3
  , "100" after 300ns      --4
  , "101" after 350ns      --5
  , "110" after 400ns      --6
  , "111" after 450ns;     --7

  m: decoder port map (ena,sel,x);

end bench;
```

3.b) Main program:

```
library IEEE;
use ieee.std_logic_1164.all;

entity decoder is
    generic( n : integer := 3);
    port (ena: in std_logic;
          sel: in std_logic_vector (n-1 downto 0);
          x : out std_logic_vector ((2**n)-1 downto 0)
        );
end decoder;

architecture generic_decoder of decoder is
begin
    process (ena,sel)
        variable temp1 : std_logic_vector(x'high downto 0);
        variable temp2 : integer range 0 to x'high;

    begin
        temp1:= (OTHERS => '1');
        temp2:=0;
        if (ena='1') then
            for i in sel'range loop
                if (sel(i)='1') then
                    temp2:=2*temp2+1;
                else
                    temp2:=2*temp2;
                end if;
            end loop;
            temp1(temp2):='0';
        end if;
        x<=temp1;
    end process;
end architecture;
```

Test-bench when generic(n : integer := 3);

```

library IEEE;
use ieee.std_logic_1164.all;

entity testdecoder is
end;

architecture bench of testdecoder is
constant n : positive := 3;
component decoder
    generic (n: integer := n);
    port (ena: in std_logic;
          sel: in std_logic_vector (n-1 downto 0);
          x : out std_logic_vector ((2**n)-1 downto 0)
        );
end component;

signal ena    : std_logic;
signal sel    : std_logic_vector (n-1 downto 0);
signal x      : std_logic_vector ((2**n)-1 downto 0);

begin


ena    <= '0', '1' after 100ns;
sel    <= "000"          --0
, "001" after 50ns       --1
, "000" after 100ns      --0
, "001" after 150ns      --1
, "010" after 200ns      --2
, "011" after 250ns      --3
, "100" after 300ns      --4
, "101" after 350ns      --5
, "110" after 400ns      --6
, "111" after 450ns;     --7

m: decoder generic map(n) port map (ena,sel,x);

end bench;

```

Waveform when generic(n : integer := 3);

 

Test-bench when generic(n : integer := 2);

```

library IEEE;
use ieee.std_logic_1164.all;

entity testdecoder is
end;

architecture bench of testdecoder is
constant n : positive := 2;
component decoder
    generic (n: integer := n);
    port (ena: in std_logic;
          sel: in std_logic_vector (n-1 downto 0);
          x : out std_logic_vector ((2**n)-1 downto 0)
        );
end component;

signal ena    : std_logic;
signal sel    : std_logic_vector (n-1 downto 0);
signal x      : std_logic_vector ((2**n)-1 downto 0);

begin


ena    <= '0', '1' after 100ns;
sel    <= "00"                --0
, "01" after 50ns              --1
, "00" after 100ns             --0
, "01" after 150ns             --1
, "10" after 200ns             --2
, "11" after 250ns             --3
, "00" after 300ns             --0
, "01" after 350ns             --1
, "10" after 400ns             --2
, "11" after 450ns;           --3

m: decoder generic map(n) port map (ena,sel,x);

end bench;

```

Waveform when generic(n : integer := 2);

 

3.c) Main program:

```
library IEEE;
use ieee.std_logic_1164.all;

entity decoder is
    generic( n : integer := 4);
    port (ena: in std_logic;
          sel: in integer range (2**n)-1 downto 0;
          x : out std_logic_vector ((2**n)-1 downto 0)
        );
end decoder;

architecture generic_decoder of decoder is
begin
    process (ena,sel)
        variable templ : std_logic_vector(x'high downto 0);

        begin
            templ:= (OTHERS => '1');
            if (ena='1') then
                templ(sel):='0';
            end if;
            x<=templ;
        end process;
    end architecture;
```

Test-bench for generic(n : integer := 4):

```
library IEEE;
use ieee.std_logic_1164.all;

entity testdecoder is
end;

architecture bench of testdecoder is
constant n : positive := 4;
component decoder
    generic (n: integer := n);
    port (ena: in std_logic;
          sel: in integer range (2**n)-1 downto 0;
          x : out std_logic_vector ((2**n)-1 downto 0)
        );
end component;

signal ena   : std_logic;
signal sel: integer range (2**n)-1 downto 0;
signal x     : std_logic_vector ((2**n)-1 downto 0);


begin

ena   <= '0'           , '1' after 100ns;
sel   <= 0 , 1 after 50ns
      , 0 after 100ns , 1 after 150ns
      , 2 after 200ns , 3 after 250ns
      , 4 after 300ns , 5 after 350ns
      , 6 after 400ns , 7 after 450ns
      , 8 after 500ns , 9 after 550ns
      , 10 after 600ns , 11 after 650ns
      , 12 after 700ns , 13 after 750ns;

m: decoder generic map(n) port map (ena,sel,x);

end bench;
```

Waveform for generic(n : integer := 4):

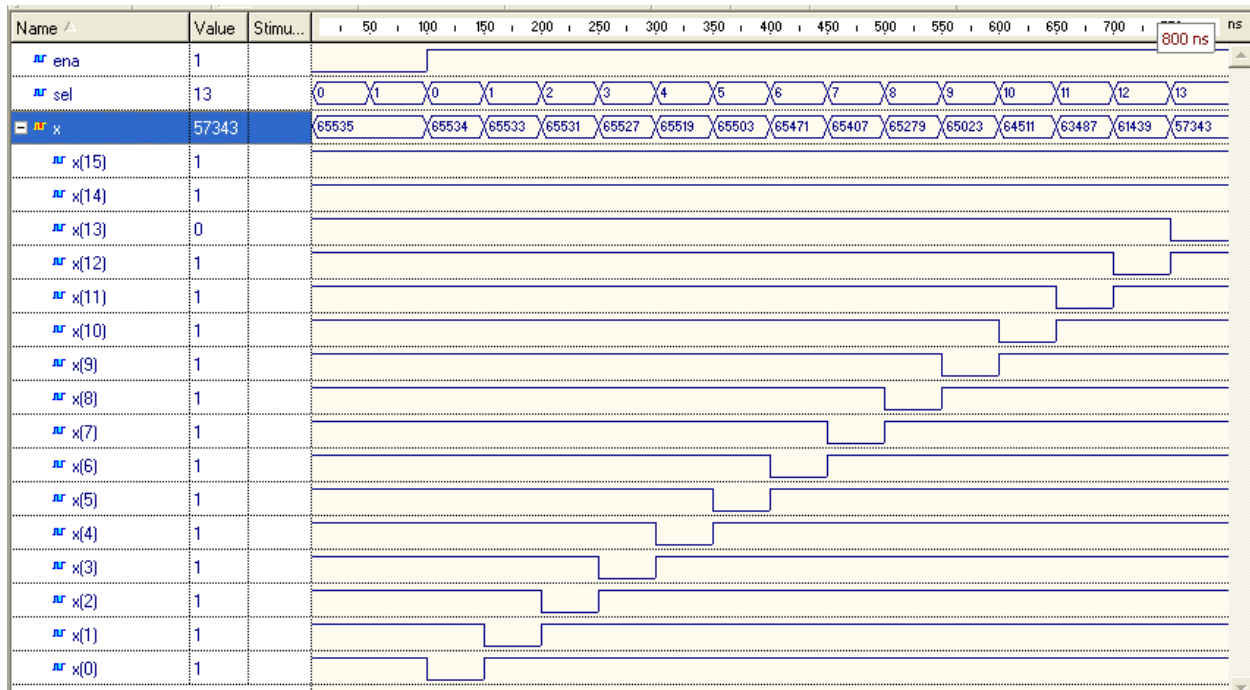

4.

List of used operators

- := , <= , XOR

List of used attributes

- input'range

List of used generics

- generic (n: integer := 7)